

UNIT - V

FLIP FLOPS

①

CLASSIFICATION OF DIGITAL CIRCUITS

Digital circuits are divided into two types. They are

a) Combinational Circuits.

b) Sequential Circuits.

COMBINATIONAL CIRCUITS

* A combinational logic is achieved by logic gates AND, OR, NOR,

X-OR, NOR, NAND and X-NOR.

* does not contain any memory element


* in combinational logic, the present O/P depends

only on present C/P combinations -

the behaviour of combinational circuit is described

by the set of O/P functions.

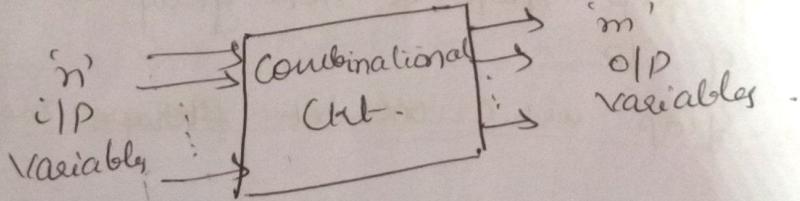Ex:- Address, Encoder, Decoder, Multiplexer, Demultiplexer.



SEQUENTIAL CIRCUITS


* A sequential logic is achieved by a memory element called flip-flop. ~~flip-flop~~ ~~with CLK (or)~~ ~~Enable~~ ~~True C/P's~~ ~~Syncronous to~~ ~~Call other E's~~

* in sequential logic, the present O/P not only depends on present C/P but also depends on previous O/P of a sequential Ckt.

The behaviour of sequential ckt described by set of O/P fun.


O/P's can be controlled irrespective of change in C/P's.

(3) COM

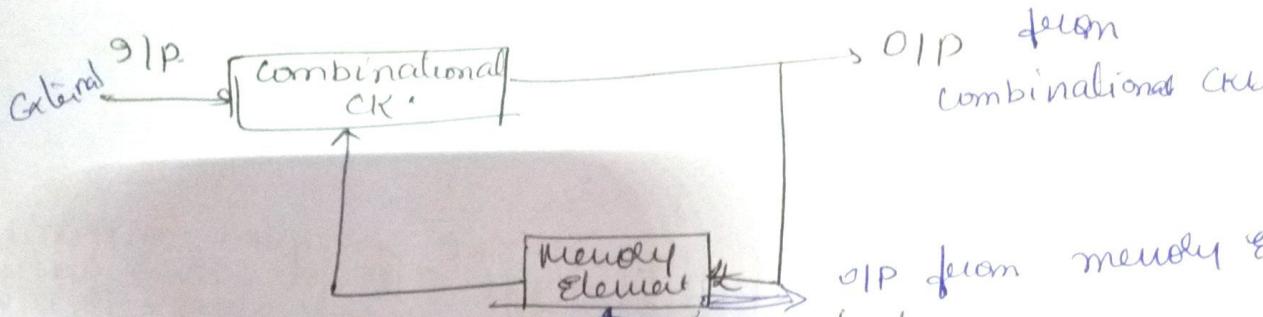

- The sequential Circuits are classified as:
 - * Synchronous Sequential Circuits → depends on clock signals can affect the memory Element only at discrete instants
 - * Asynchronous Sequential Circuits → it does not have clk. of time → change in i/p signals can effect memory Element at any instant of time.

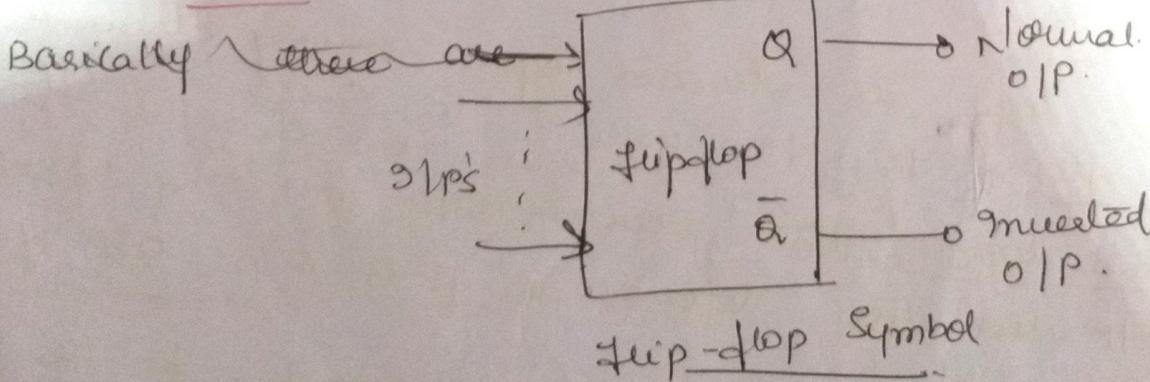- The memory Element used in sequential Circuits are flip-flops.
- FLIP-FLOPS → O/P changes only when we apply CLK & enable
- flip flop has two possible stable states & these states are identified as logic '1' and logic '0'.
- The O/P of flip-flop is not going to change even after removal of i/p.
- Hence flip-flop is a one-bit storage memory Element & device.



- Basically there are four flip-flops, they are
 - 1) SR flip flop
 - 2) JK flip flop
 - 3) D flip flop
 - 4) T flip flop.

ICL

→ O/P changes for a small change
in the I/P.

A circuit which can indefinitely store a logic '1' or a logic '0' is called the basic - bi stable Element.

* A latch is an example of basic - bi stable Element.

- The latch means the information is locked &
latched in the Ckt.

- A latch is the most basic type of flip flop.

- It can be constructed using NAND or NOR gates.

- According to the latch are of 2 types.


1) NAND latch gate latch.

2) NOR gate latch.

S - SET

R - RESET


b) using NAND gate

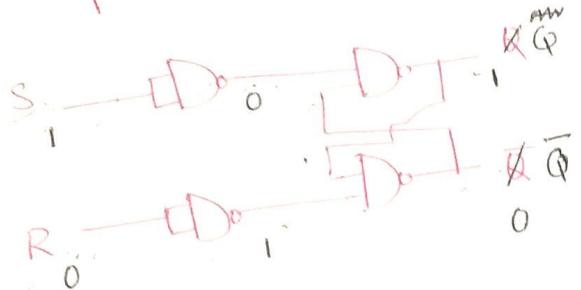

Truth table

Inputs		Outputs
S	R	Q & \bar{Q}
0	0	No change
0	1	set 0 → 1
1	0	reset 1 → 0
1	1	Not allowed


Case i) when $S=0$ and $R=0$

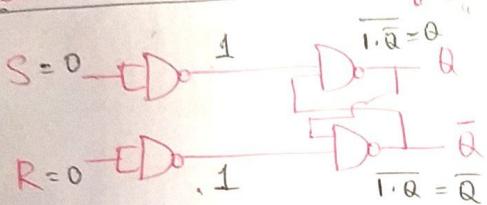

any
1. (a) - any


2. When $S=0$ & $R=0$, then $Q=Q$ and $\bar{Q}=\bar{Q}$.

Case ii) when $S=0$ and $R=1$

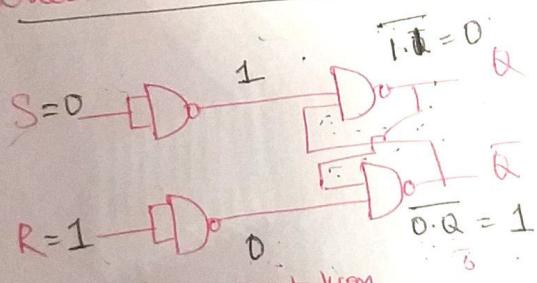


∴ When $S=0$ & $R=1$, then $Q=0$ & $\bar{Q}=1$

Case iii) when $S=1$ & $R=0$

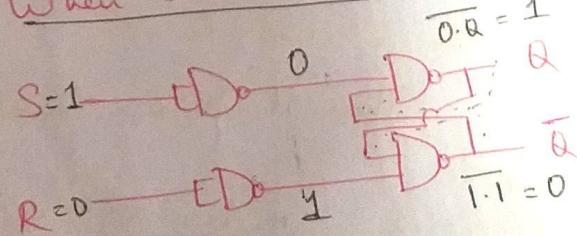

∴ When $S=1$ & $R=0$, then $Q=1$ and $\bar{Q}=0$

case - I

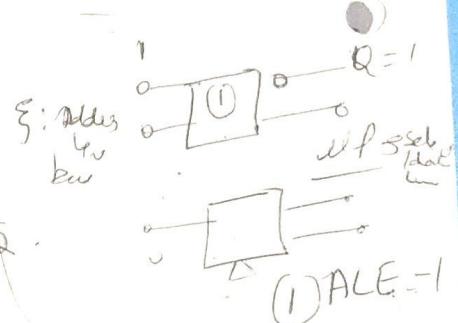


SOH



10000000

0000001

A/D Multi

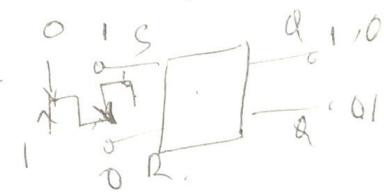

↑ ↓

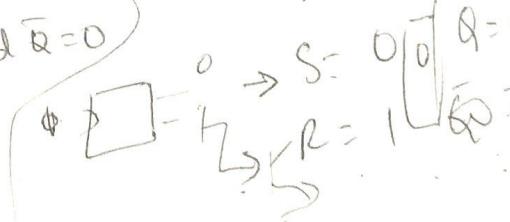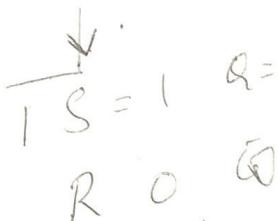


S=1

$\overline{Q} = 0$ (Set)

R=1 $\overline{Q} = 1$ (Reset)


∴ When $S=1 \wedge R=1$, then Output is invalid

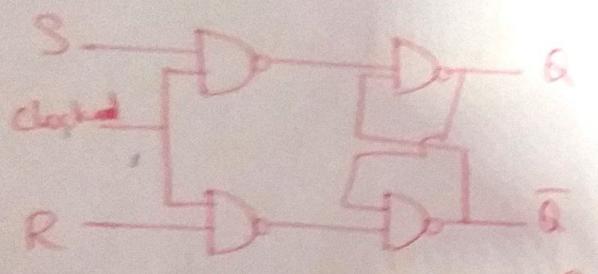SR Flip Flop: with positive edge triggered logic




Truth Table			
Inputs	Outputs	Notes	
$S = 0$	$Q = 0$	Initial state	
$S = 1$	$Q = 0$	Set	
$R = 1$	$Q = 1$	Reset	
$S = 0$	$Q = 1$	Keep State	
$S = 1 \wedge R = 1$	Invalid	Indeterminate	

Case i) when $S=0 \wedge R=0$,

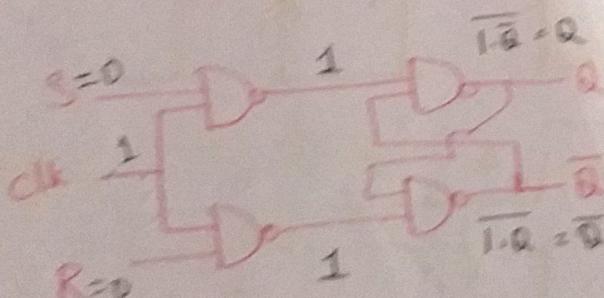


∴ when $S=0 \wedge R=0$, then $Q=0$ and $\overline{Q}=1$

Case ii) when $S=0 \wedge R=1$,

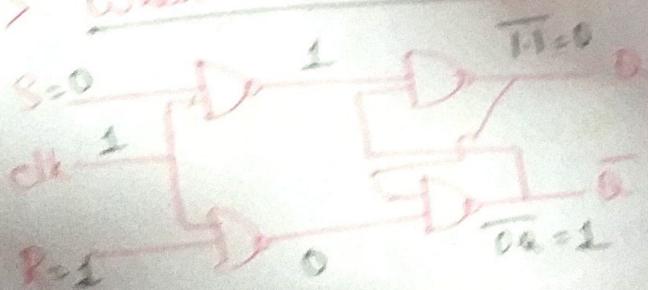



∴ when $S=0 \wedge R=1$,
then $Q=0 \wedge \overline{Q}=1$

Case iii> When $S=1$ & $R=0$,

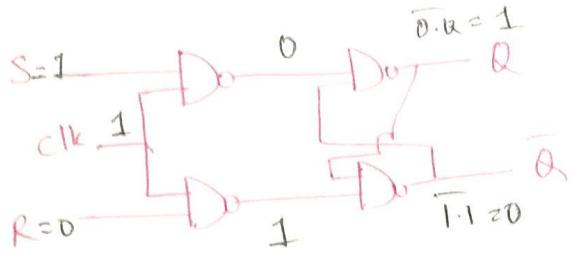


\therefore when $S=1$ & $R=0$, then $Q=1$ & $\bar{Q}=0$.

Case iv> When $S=1$ & $R \neq 1$

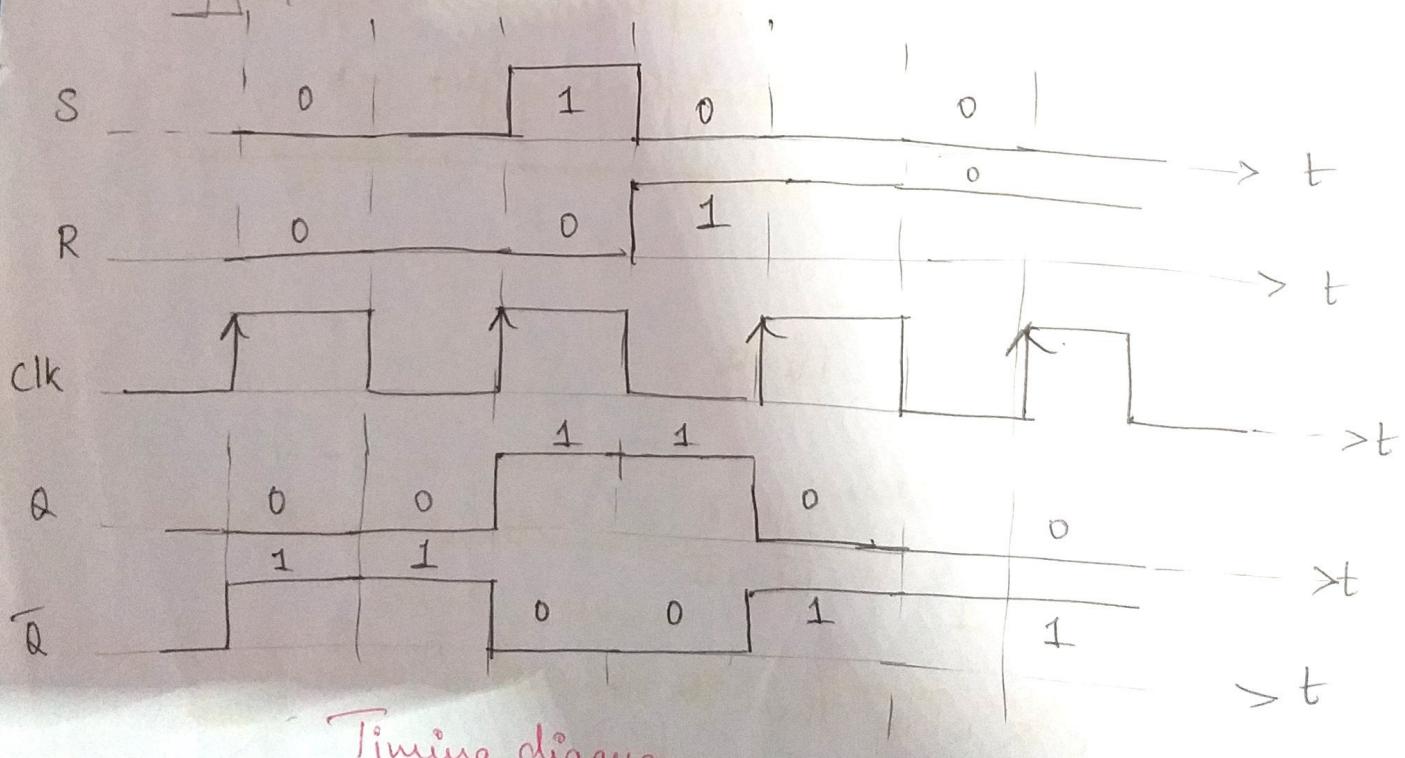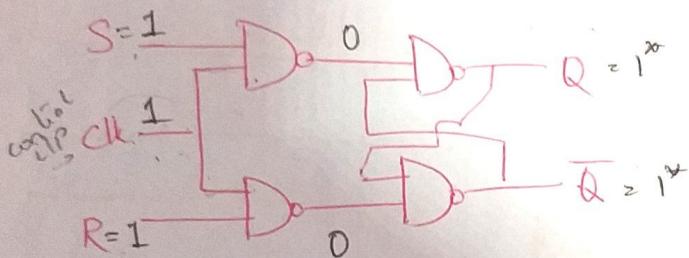

Timing diagram

flip-flop and its applications

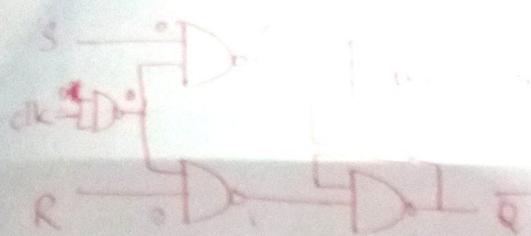

Truth table	
Clk	0
S	0
R	0
D	0
Q	0
Q̄	1
Clk	1
S	0
R	0
D	1
Q	1
Q̄	0
Clk	1
S	1
R	0
D	0
Q	0
Q̄	1
Clk	1
S	1
R	1
D	0
Q	0
Q̄	1
Clk	1

Applications of flip-flops:

1. It is used as a memory element
2. In digital circuits flip flop is used to eliminate key debouncing
3. Counters & registers are constructed using flip flop
4. In digital logic flip-flop can be used as a delay element

Comparison b/w combinational & Sequential circuit

Combinational circuit

1. Only logic gates
2. It depends only on present inputs.
3. Is used to realize boolean expression.
4. ex. half adder, full adder, decoders, encoders

Sequential circuit

- combinational circuit and a memory device .
- It depends on present and previous outputs .
- It is used to record number of events .
- counters , shift registers etc .

The sequential circuits are classified as,

- Synchronous sequential circuits - signals can affect n. element only at discrete time
- Asynchronous sequential circuits
↳ change in input signals can affect memory elements at any instant of time


The memory element used in sequential circuits are flip-flops which is capable of storing one bit binary information.

Basically there are four flip-flops:

- 1) SR flipflop
- 2) JK flipflop
- 3) D flipflop
- 4) T flipflop

R-S latch

a) R-S latch using NOR gate

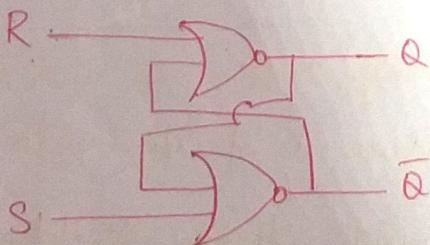


Truth table

Inputs	Outputs		
S	R	Q	\bar{Q}
0	0	No change	
0	1	0	1
1	0	1	0
1	1	Not allowed	

(6)


When both $R=0$ & $S=0$, then

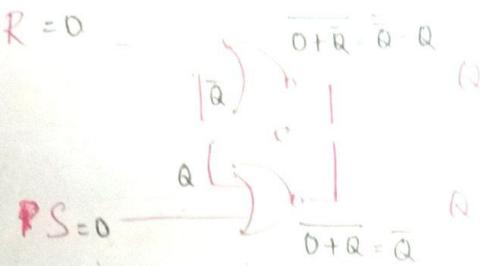

latch


i.e. When $R=0$ & $S=0$, the output of flip flop remains same

Case ii) When $R=1$ & $S=0$, then

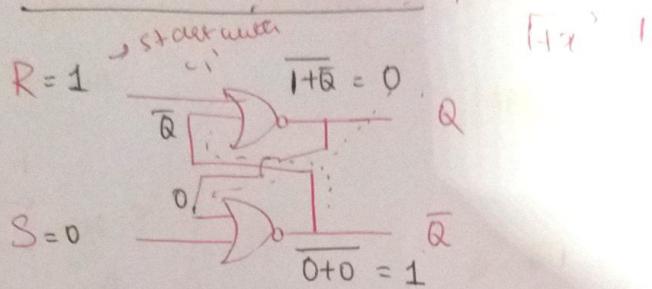

i.e. when $R=1$ and $S=0$, the output Q is zero & \bar{Q} is one

Case iii) When $R=0$ & $S=1$, then

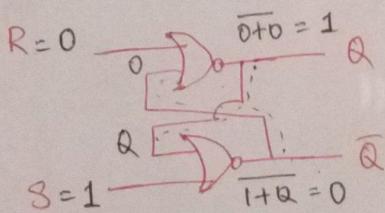

i.e. when $R=0$ and $S=1$, the output Q is one and \bar{Q} is zero.

Case iv) When $R=1$ and $S=1$, then

