


## CMOS WORKING PRINCIPLE AND APPLICATIONS

for "Complementary Metal Oxide Semiconductor". CMOS technology is one of the most popular technology in the computer chip design industry and broadly used today to form integrated circuits in numerous and varied applications. Today's computer memories, GPUs and cell phones make use of this technology due to several key advantages. This technology makes use of both P channel and N channel semiconductor devices.

One of the most popular MOSFET technologies available today is the Complementary MOS or CMOS technology. This is the dominant semiconductor technology for microprocessors, microcontroller chips, memories like RAM, ROM, EEPROM and application specific integrated circuits (ASICs).
 
### CMOS (Complementary Metal Oxide Semiconductor)

The main advantage of CMOS over NMOS and BIPOLAR technology is the much smaller power dissipation. Unlike NMOS or BIPOLAR circuits, a Complementary MOS circuit has almost no static power dissipation. Power is only dissipated in case the circuit actually switches. This allows integrating more CMOS gates on an IC than in NMOS or bipolar technology, resulting in much better performance. Complementary Metal Oxide Semiconductor transistor consists of P-channel MOS (PMOS) and N-channel MOS (NMOS). Please refer the link to know more about the fabrication process of CMOS transistor.



CMOS Transistor

### NMOS


NMOS is built on a p-type substrate with n-type source and drain diffused on it. In NMOS, the majority carriers are electrons. When a high voltage is applied to the gate, the NMOS will conduct. Similarly, when a low voltage is applied to the gate, NMOS will not conduct. NMOS are considered to be faster than PMOS, since the carriers in NMOS, which are electrons, travel twice as fast as the holes.



NMOS Transistor
 
### PMOS

P-channel MOSFET consists P-type Source and Drain diffused on an N-type substrate. Majority carriers are holes. When a high voltage is applied to the gate, the PMOS will not conduct. When a low voltage is applied to the gate, the PMOS will conduct. The PMOS devices are more immune to noise than NMOS devices.




PMOS Transistor

## CMOS Working Principle

In CMOS technology, both N-type and P-type transistors are used to design logic functions. The same signal which turns ON a transistor of one type is used to turn OFF a transistor of the other type. This characteristic allows the design of logic devices using only simple switches, without the need for a pull-up resistor.

In CMOS logic gates a collection of n-type MOSFETs is arranged in a pull-down network between the output and the low voltage power supply rail ( $V_{ss}$  or quite often ground). Instead of the load resistor of NMOS logic gates, CMOS logic gates have a collection of p-type MOSFETs in a pull-up network between the output and the higher-voltage rail (often named  $V_{dd}$ ).

 
Thus, if both a p-type and n-type transistor have their gates connected to the same input, the p-type MOSFET will be ON when the n-type MOSFET is OFF, and vice-versa. The networks are arranged such that one is ON and the other OFF for any input pattern as shown in the figure below.



CMOS Logic Gate using Pull-Up and Pull-Down Networks


CMOS offers relatively high speed, low power dissipation, high noise margins in both states, and will operate over a wide range of source and input voltages (provided the source voltage is fixed). Furthermore, for the better understanding of the Complementary Metal Oxide Semiconductor working principle, we need to discuss in brief about CMOS logic gates as explained below.

### CMOS Inverter

 



 The circuit shown in the figure below, it consists of ~~PMOS and NMOS transistors~~ with input A and output Y.




CMOS Inverter

The NMOS transistor has an input from Vss (ground) and PMOS transistor has an input from Vdd. The terminal Y is output. When a high voltage ( $\sim V_{dd}$ ) is given at input terminal (A) of the inverter, the PMOS becomes open circuit and NMOS switched OFF so the output will be pulled down to Vss. When a low-level voltage ( $< V_{dd}$ ,  $\sim 0v$ ) applied to the inverter, the NMOS switched OFF and PMOS switched ON. So the output becomes Vdd or the circuit is pulled up to Vdd.

INPUT	LOGIC INPUT	OUTPUT	LOGIC OUTPUT
0 v	0	Vdd	1
Vdd	1	0 v	0
 
### CMOS NAND Gate

The below figure shows a 2-input Complementary MOS NAND gate. It consists of two series NMOS transistors between Y and Ground and two parallel PMOS transistors between Y and VDD.




CMOS NAND Gate

If either input A or B is logic 0, at least one of the NMOS transistors will be OFF, breaking the path from Y to Ground. But at least one of the pMOS transistors will be ON, creating a path from Y to VDD. Hence, the output Y will be high. If both inputs are high, both of the nMOS transistors will be ON and both of the pMOS transistors will be OFF. Hence, the output will be logic low. The truth table of NAND logic gate given in below table.

an Network		Network	T Y
0	0	OFF	1
0	1	OFF	1
1	0	OFF	1
1	1	ON	0
 
### CMOS NOR Gate

A 2-input NOR gate is shown in the figure below. The NMOS transistors are in parallel to pull the output low when either input is high. The PMOS transistors are in series to pull the output high when both inputs are low, as given in below table. The output is never left floating.



Complementary MOS NOR Gate

The truth table of NOR logic gate given in below table.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

### CMOS Applications

Complementary MOS processes were widely implemented and have fundamentally replaced NMOS and bipolar processes for nearly all digital logic applications. The CMOS technology has been used for the following digital IC designs.

- Computer memories, CPUs
- Microprocessor designs
- Flash memory chip designing
- Used to design application specific integrated circuits (ASICs)

I believe that you have got a better understanding of this concept. Furthermore, any queries regarding this concept or electronics projects, please give your valuable suggestions by commenting in the comment section below.

Here is a question for you, why CMOS is preferable than NMOS?