


OPERATIONAL AMPLIFIER [OP-AMP]

July 11

What is an operational amplifier.

- An operational amplifier (or) op-amps, is a direct coupled multistage voltage amplifier with an extremely high gain.
 - Its behaviour can be controlled by adding a suitable feed back.
 - It has a very high input impedance.
 - a very low output impedance.
 - The early op-amps were mainly used for performing mathematical operations such as addition, subtraction, multiplication, differentiation, and integration.
 - Hence the device got the name operational amplifier.
- Nowadays op-amps are used for coupling amplification, impedance matching, delay elements, buffer etc.

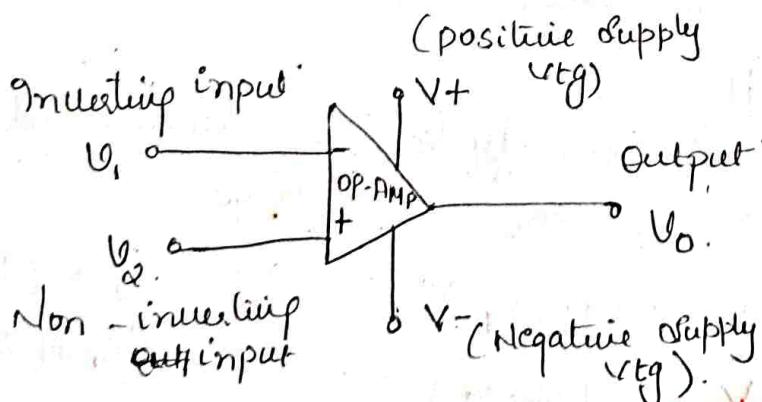CIRCUIT SYMBOL OF AN OPAMP AND ITS TERMINALS



Circuit Symbol for an op-amp

- Fig shows the circuit symbol of an op-amp.
- There are five main terminals, namely:
 1. A Non-inverting i/p terminal denoted by '+' symbol.
 2. An inverting i/p terminal denoted by '-' symbol.
 3. An o/p terminal.
 4. A positive supply voltage terminal denoted by V_T .
 5. A negative supply voltage terminal denoted by V_B .

V_1 = Voltage at the inverting input.
 V_2 = Voltage at the Non-inverting input.
 V_o = Output Voltage.

- All these voltages are measured with respect to ground.
- Normally, the op-amp operates from a bipolar dual power supply i.e., two power supplies.
- One positive & one negative with a common ground terminal.
- The supply voltages are denoted by V^+ & V^- and they are in the range $\pm 9V$ to $\pm 22V$.
- They are typically $\pm 15V$.
- A voltage applied to the non-inverting input produces an in-phase (or) same polarity V_{tg} at O/P.
- While a voltage applied to the inverting input produces an out-of-phase (or) opposite polarity V_{tg} at the O/P.
- The O/P V_{tg} denoted by V_o is proportional to the difference b/w the O/P voltages.

$$\text{i.e., } V_o \propto (V_2 - V_1)$$

$$V_o = A(V_2 - V_1)$$

$$(a) \quad V_o \propto (V_p - V_n)$$

$$V_o = A(V_p - V_n)$$

where $A \Rightarrow$ proportionality constant & which is equal to gain of the differential amplifier.

$$\text{A} = \text{voltage gain.}$$

hence, Op-Amp is basically a differential (δ) differential amplifier.

OPERATION OF AN - OPAMP [ideal - op-amp].

The op-Amp is basically a differential amplifier which amplifies the difference b/w its two i/p voltages.

$$V_o = A V_d = A [V_2 - V_1]$$

where $V_d = [V_2 - V_1] = \text{differential or difference i/p voltage.}$
 $A = \text{open-loop voltage gain.}$


when a voltage V_1 is applied to the inverting i/p with the non-inverting i/p grounded [$V_2 = 0$] the o/p voltage is

$$V_o = A [V_2 - V_1]$$

$$V_o = A [0 - V_1]$$

$$\boxed{V_o = -AV_p}$$

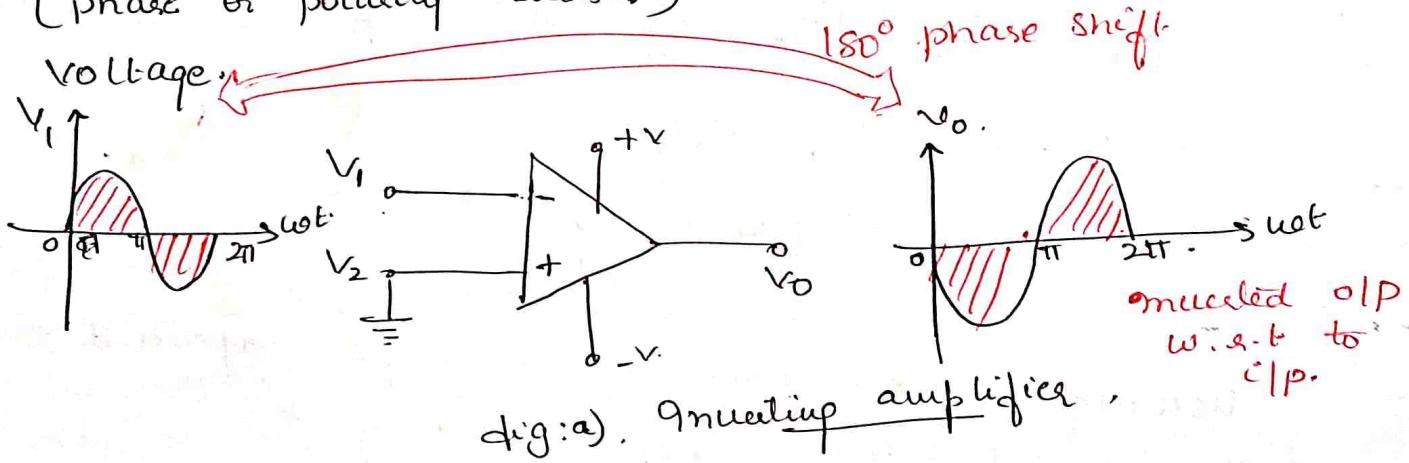This indicates that the o/p voltage will be inverted (phase or polarity reversed) with respect to the input



On the other hand, when a voltage is applied to the Non-Inverting amplifier input with the inverting input grounded ($V_1 = 0$) the o/p voltage is

$$V_o = A [V_2 - 0]$$

$$\boxed{V_o = AV_2}$$

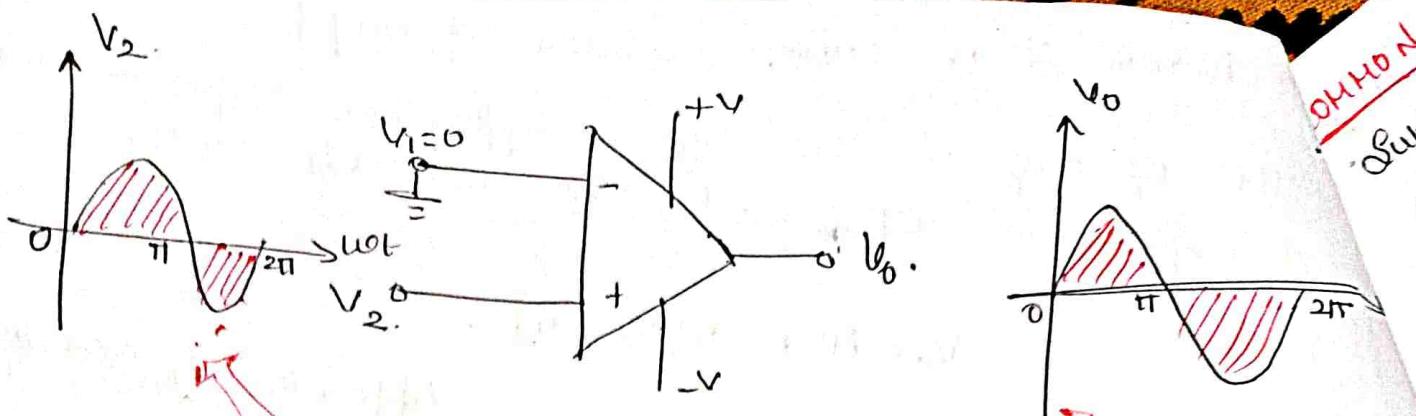


Fig. b Non-inverting amplifier.

zero phase shift

Fig a & b : Shows basic operation of an op-amp

① DIFFERENTIAL GAIN: (A_d)

- Since the differential amplifier amplifier the difference b/w two input ^(voltages) signals & hence gain provided under this condition is called differential gain.

$$\text{W.R.T "From Eqn"} \quad V_o = A [V_2 - V_1]$$

where A_d is differential gain

Let $V_d = [V_2 - V_1]$ is differential voltage

$$\therefore V_o = A_d V_d$$

$$A_d = \frac{V_o}{V_d}$$

Usually the gain is always expressed in terms of decibels (dB) i.e.,

$$\begin{aligned} A_d(\text{dB}) &= 20 \log_{10} \left(\frac{V_o}{V_d} \right) \\ &= 20 \log_{10} (A_d). \end{aligned}$$

COMMON MODE GAIN (AC).

(3)

Suppose the two i/p signals given to the two i/p terminals of differential amplifier, are which are equal in all respect that is equal amplitudes, equal frequencies and equal in phase, then the o/p of ideal differential amplifier is equal to zero.

$$\therefore V_o = A_c [V_2 - V_1] \quad \text{But } V_1 = V_2 \rightarrow \text{Same vctg applied}$$

$$\therefore V_o = 0$$

- But the o/p voltages of practical amplifier not only depend on the difference b/w two i/p voltages, but also depends on the average common lead of the two i/p signal.
- Pract. average lead of the two i/p signals is called common-mode signal and is denoted as V_C .

- practically, the differential amplifier produces the common mode signal output voltage proportional to the gain with which it amplifies the common mode signal to produce the o/p is called common mode gain denoted as ' A_c ' and is given by

$$V_o = A_c V_C$$

$$\boxed{\therefore A_c = \frac{V_o}{V_C}}$$

The total o/p vfg of any differential amp
Expressed as sum of o/p vfg under differential &
& o/p vfg under common mode.

$$V_o = Ad \frac{V_d}{V_d} + Ac V_c$$

COMMON mode Rejection Ratio (CMRR)

- CMRR is the ability of differential amplifier to reject a common mode signal.
- the CMRR is defined as the ratio of differential mode gain to the common mode gain.
It is denoted as ' ρ '
- As W.K.T for ideal differential amplifier $Ad = \infty$ & $Ac = 0$.

$$CMRR = \rho = \left| \frac{Ad}{Ac} \right|$$

- ∵ Hence the CMRR is also equal to infinity.
- Many a. time CMRR is defined as $CMRR (dB) = 20 \log_{10} \left| \frac{Ad}{Ac} \right| dB$.

PIN DIAGRAM OF OP-AMP IC 741 & ITS SIGNIFICANCE:

why it's named as 741 IC.
[out of 8 pins]

- 7 means 7 pins are connected. see in the next page.
 - 4 are considered as o/p i.e., two o/p's & two are supply voltages.
 - 1 is o/p pin
 - 2 pins are offset null.
- ∴ it is named as 741 IC.

(4).

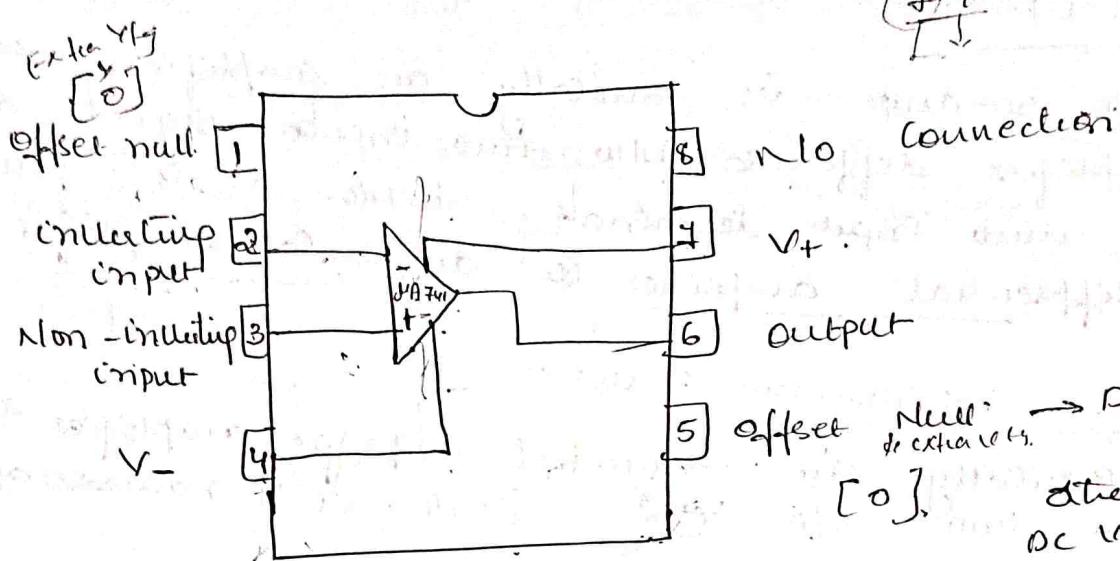


Fig.: pin diagram of IC 741.


- An integrated circuit (IC) is an electronic circuit which all the components such as transistors, resistors etc., are produced and interconnected during the manufacturing process on a single piece of silicon wafer called a chip.
- A very popular and widely used IC version of Op-Amp is μA741, which is 8 pin IC available in dual-in-line package (DIP).
- The pin diagram of μA741 is as shown in Fig. Pin 1 & 5 are used to null or balance the offset voltages. [offset voltages is the DIP terminal. Even when both the inputs are zero, the output voltage that occurs is not zero].
- Pin 2 is the inverting input terminal.
- Pin 3 is the non-inverting input pins.
- Pin 4 & 7 are the supply voltage pins. ['+' to pin '2' & '-' to pin 4].
- Pin 5 is the DIP terminal. No connection is made.

IDEAL OP-AMP:

- An op-amp is basically an amplifier which amplifies different signals applied at its two input terminals, hence it is called a differential amplifier (or) differential amplifier

IDEAL DIFFERENTIAL AMPLIFIERS

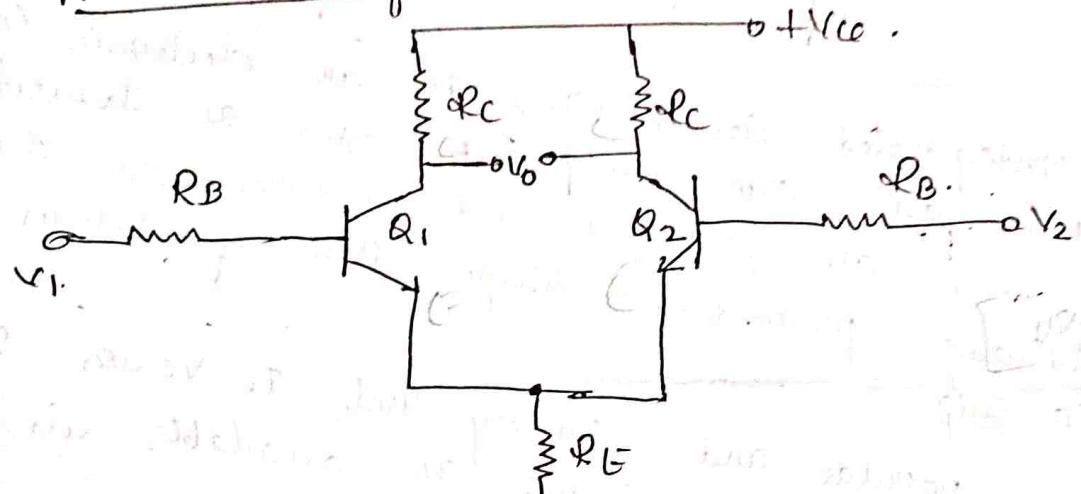- Basically the differential amplifier amplifies the difference b/w two i/p vts. Hence it is named as differential amplifier.




diga; $-V_{EE}$

- Let us consider differential operated ckt is shown in fig (a).

- The ckt consists of two transistors connected back-to-back as shown in the fig (a)

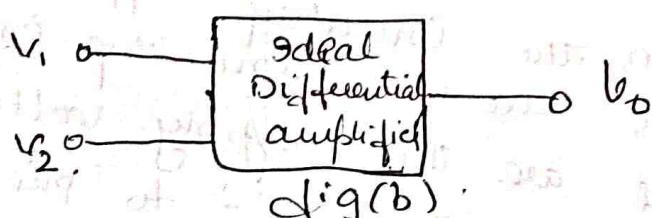For the two i/p's are given to the base of each transistor and o/p is taken b/w two collectors of two transistors.



- Fig shows the symbolic representation of differential amplifier.

~~recess~~ ~~gained~~ v_1 and v_2 are the two i/p voltages and v_o is the o/p v/tg.

Q. In an ideal differential amplifier the o/p v/tg is directly proportional to difference b/w two i/p voltages.

$$\text{i.e., } V_o \propto (v_2 - v_1)$$

$$V_o = A(v_2 - v_1)$$

A = proportionality const and which is equal to gain of the differential amplifier.

PROBLEM:

1. For a differential amplifier with input voltage are 600μV and 480μV. The differential gain of the amplifier is 10,000. Find the output voltage for CMRR = 10⁸. (differential gain)

Soln Given that $v_1 = 600\mu V$, $v_2 = 480\mu V$ and $A_d = 10000$

i) For $\text{CMRR} = 200$,

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|$$

$$200 = \frac{10000}{A_c}$$

$$\therefore A_c = \frac{10000}{200} = 50$$

$$V_c = \frac{v_1 + v_2}{2} = \frac{600\mu V + 480\mu V}{2}$$

$$\boxed{V_c = 540\mu V}$$

$$\text{Hence } V_d = v_1 - v_2 = 600\mu V - 480\mu V = 120\mu V$$

∴ The o/p v/tg of a differential amplifier is given by

$$V_o = A_d V_d + A_c V_c$$

$$V_o = 10000 \times 120 \times 10^{-6} + 50 \times 540 \times 10^{-6}$$

$$V_o = 1.22 + mV \quad \text{or} \quad 1.227V$$

$$\text{ii) } CMRR = 10^8$$

$$\therefore A_c = \frac{A_d}{CMRR} = \frac{10000}{10^8} = \underline{10^{-4}}$$

$$V_c = 540 \mu V$$

$$V_d = \underline{120 \mu V}$$

O/P v_c

$$V_o = A_d V_d + A_c V_c$$

$$V_o = 10000 \times 120 \times 10^{-6} + 10^{-4} \times 540 \times 10^{-6}$$

$$V_o = \underline{1.2 V}$$

- ② An op-amp has a differential gain of 500 and a CMRR of 80dB. If the common mode i/p signal is $2 \sin 100\pi t V$, calculate the common-mode o/p v_c

Ques^n

$$CMRR \text{ in dB} = 20 \log \left| \frac{A_d}{A_c} \right|$$

$$\text{i.e. } 80 \text{ dB} = 20 \log \left| \frac{A_d}{A_c} \right|$$

$$\text{or } \frac{A_d}{A_c} = \text{antilog} \left(\frac{80}{20} \right) = \text{antilog}(4)$$

$$\therefore \frac{A_d}{A_c} = 10000$$

$$\text{(Q1)} \quad A_c = \frac{A_d}{10000} = \frac{500}{10000} = \underline{0.05}$$

O/P v_c of common-mode o/p v_c

$$\boxed{A_c V_c = 0.05 \times 2 \sin 100\pi t .}$$

CHARACTERISTICS OF AN IDEAL OP-AMP.

(5)

(6)

- An ideal op-amp does not draw any current from the voltage sources connected to its o/p terminal. thus its input resistance is infinite i.e., $R_i = \infty$.
2. The o/p $V_{O/P}$ of an ideal op-amp is independent of the current drawn from it. This means that o/p has zero o/p resistance i.e., $R_o = 0$. \rightarrow [o/p $V_{O/P}$ is high].
 3. The voltage gain of an ideal op-amp is infinite, $A = \infty$. This implies that, for a given o/p voltage, the differential input voltage is essentially zero.
 4. An ideal op-amp amplifies signals of any frequency with a constant gain, which implies that o/p has an infinite bandwidth, $B.W.L = \infty$.
 5. When equal voltages are applied to both the inputs of an ideal op-amp, its output voltage is zero. Thus, it has a perfect balance.
 6. The common-mode rejection ratio of an ideal op-amp is infinite. i.e., $CMRR = \infty$.
 7. An ideal op-amp has infinite slew-rate i.e., $SR = \infty$. This implies that the o/p voltage change simultaneously with the i/p voltages.
 8. The characteristics of an ideal op-amp do not change with temperature.
 9. The supply voltage (or) power supply rejection ratio of an ideal op-amp is zero, i.e., $PSRR = 0$.

CHARACTERISTICS OF PRACTICAL OP-AMPS are:

PRACTICAL (a) non - ideal op-Amps differs from the IDEAL
The Characteristics are:

1. The open-loop voltage gain is not infinite, but is generally in the range of 10^4 to 10^6 (or) more.
2. The C/I/P resistance is not infinite, but is higher of the order of megaohms.
3. The output resistance is not zero, but is of the order of 100Ω or less.
4. The B.W is not infinite, but is in the range of 1 to 100 MHz.
5. The common-mode rejection ratio is not infinite, but is of the order of 90dB.
6. The +ve & -ve voltage swings (O/I/P voltages) are limited by the supply voltages namely, V_+ & V_- .

COMPARISON B/W IDEAL & PRACTICAL OPAMP:

NO	PARAMETER	SYMBOL	IDEAL VALUE	PRACTICAL VALUE
1.	Open loop voltage gain	A & (A_{OL})	∞	Typical value for 741 is 2×10^5 (max)
2.	Input resistance (impedance)	R_i	∞	Only for open loop op-amps
3.	O/I/P resistance	R_o	0	$2 M\Omega$ [100M Ω] $75\Omega \rightarrow$ (min) (1 Ω)
4.	O/I/P offset current	I_{IO}	0	$20nA$ [0.1nA]
5.	C/I/P Bias current	I_B	0	$80nA$ [100nA]
6.	C/I/P offset voltage	V_{IO}	0	$2mV$ [1mV].
7.	Common-mode rejection ratio	CMRR, P	∞	90dB
8.	Band width	B.W	∞	1MHz (at unity gain)
9.	Slew-rate	SR	∞	$0.5V/\mu s$
10.	power supply rejection ratio	PSRR	0	$30\mu V/V$ (20 $\mu V/V$)

IDEAL CHARACTERISTICS [derivations]

Infinite voltage gain ($A_{OL} = \infty$)

- Since for an ideal op-amp the differential O/P ($V_d = V_2 - V_1 = 0$). V_d is zero with a very small O/P vdg i.e.,

$$A_{OL} = \frac{\text{Infinite O/P vdg}}{\text{zero difference vdg}} = \frac{V_o}{V_d} = \frac{V_o}{0} = \infty$$


$\therefore A_{OL} = \infty$

Note: A_{OL} is also called open loop gain

b) Infinite input impedance (Resistance) ($R_i = \infty$)

- Even if we apply two c/p signals to two input terminals, the current drawn at the c/p terminal is zero. i.e., $I_1 = I_2 = 0$. It indicates the inverting & non-inverting terminals are open circuited, hence open circuit impedance is very high & it is approximate as ∞ .

W for ideal op-amp.

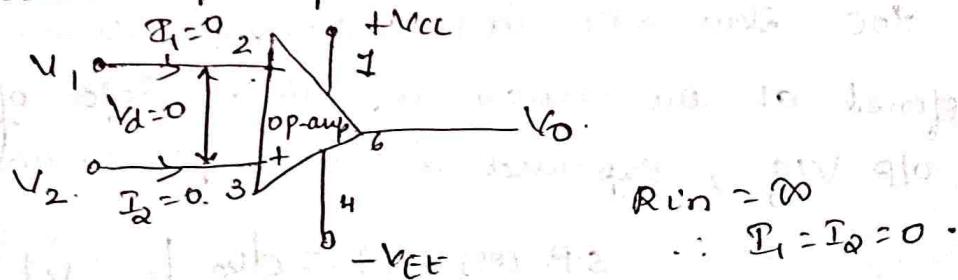

c) Zero output impedance ($Z_o = 0$):

- The O/P impedance of an ideal op-amp is zero. This ensures that the O/P vdg of op-amp remains same irrespective of the load resistance connected at the O/P terminal.

d) Input off-set Voltage ($V_{ios} = 0$)

The presence of small o/p voltage even when the i/p voltages are at ground potential (0V) zero.

i.e., $V_1 = V_2 = 0$ is called as off set voltage

$$\boxed{V_{ios} = 0}$$

e) Infinite Bandwidth ($B.W = \infty$)

It is the range of frequencies over which the amplifiers performance is satisfactory.

The B.W for ideal opamp is ∞ .

f) CMRR (P)

- It is the ratio of differential mode gain to common mode gain

$$\boxed{P = \infty}$$


$$CMRR(s) = \frac{A_d}{A_c}$$

g) Slew Rate :

The slew rate (SR) maximum slew-rate of the op-amp is defined as the maximum ~~rise~~ rate of change change of its o/p vrtg, expressed in volts per microsecond.

$$SR \text{ or } MGR = \frac{dv_o}{dt} \Big|_{\max} \text{ V / } \mu\text{sec}$$

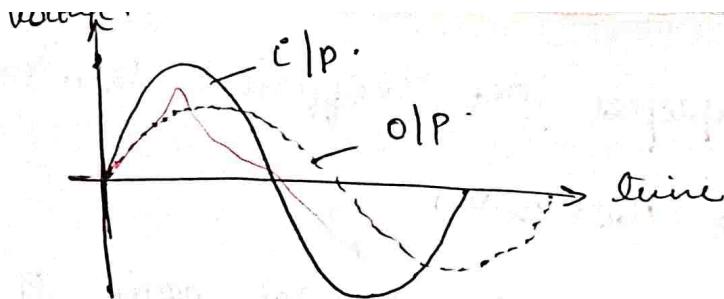- Slew-rate is a measure of how fast the op-amp's output can change in response to changes in the input signal.
- It limits the maximum operating frequency.
- If the frequency of the input signal exceeds a particular value then the output will not be able to follow the i/p faithfully & the o/p waveform will be distorted. The o/p in such situation is referred to as the slew-rate limited o/p.



Dig.: Effect of slew rate.

power supply rejection ratio ($PSRR=0$)

- The PSRR is defined as the ratio of change in c/p off-set voltage due to change in any one supply voltage by keeping other as const.
- The PSRR is also called power supply sensitivity.
- we are using two biasing voltages $+V_{CC}$ and $-V_{EE}$.
- PSRR is expressed as


$$PSRR = \frac{\Delta V_{COS}}{\Delta V_{CC}} \Big|_{V_{EE}=\text{const}}$$

$$(Q) PSRR = \frac{\Delta V_{COS}}{\Delta V_{EE}} \Big|_{V_{CC}=\text{const.}}$$

- PSRR is expressed in terms of mV/mV or MV/mV and it is zero for ideal op-amp.

PRACTICAL OP-AMP CHARACTERISTICS.

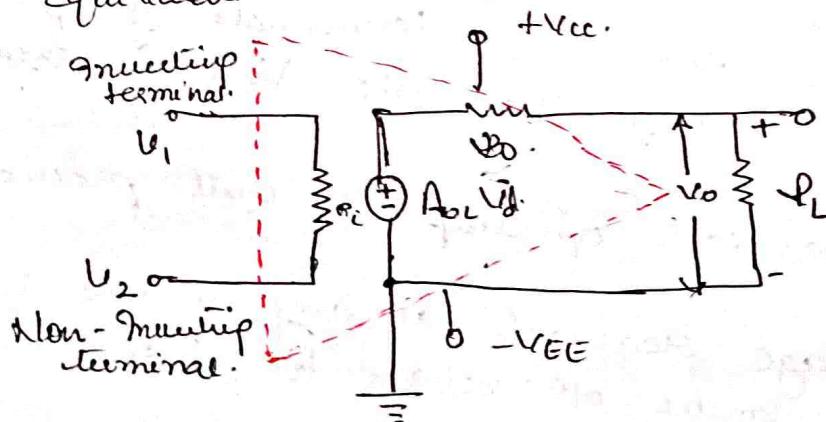for practical considerations the op-amp is replaced by its equivalent circuit as shown below



1. **Op-amp amplifies the difference b/w two signals.**

$$V_o = A_{OL} V_d = A_{OL} (V_2 - V_1)$$

INPUT
S/

1. **Open loop gain (A_{OL}):** It is the voltage gain of the op-amp with no feedback element connecting b/w i/p to o/p terminals. practically it is several thousands.
2. **Input impedance (R_i) (R_i):** - It is the impedance looking from i/p terminals of op-amp.
 - It is a finite value typically $1\text{M}\Omega$. when we design op-amps with transistors and it may be several hundred $\text{M}\Omega$ when we design with FET's.
3. **Output impedance (R_o):** - It is the impedance looking from o/p terminals of op-amp.
 - It is typically few hundred Ohms.
 - with the help of 've' feedback, it can be reduced to a very small value like 1 or 2 Ω 's.
4. **Bandwidth (B_w):** - the Bandwidth of an practical op-amp under open loop configuration is very small.
 - with the help of 've' feedback it can be increased to desired value.
5. **Input offset value:**
 - whenever both the i/p terminals of op-amp are grounded, ideally the o/p voltage should be zero.
 - But for the practical op-amp it will provide a small o/p V_{of} .
 - the o/p voltage required at any of the i/p terminals to make this small o/p voltage to zero is called i/p offset voltage.
 - Normally voltage required is in millivolt.
 - the i/p offset voltage depends on temperature.

INPUT BIAS CURRENT: (I_b)

- As we see the i/p bias current is defined as the average of two i/p currents.

$$I_b = \frac{|I_{b1}| + |I_{b2}|}{2}$$

input offset current (I_{ios})

- The difference between two inputs currents is called input offset current.


$$I_{ios} = I_{b2} - I_{b1}$$

PSRR: It is defined as the ratio of the change in the o/p offset V_{o/p} due to the change in the power supply V_{cc} keeping the other power supply V_{EE} constant.

$$PSRR = \frac{\Delta V_{ios}}{\Delta V_{cc}} \quad | \text{ const } V_{EE}$$

q) Slew Rate: [Same explanation of ideal]

BLOCK DIAGRAM OF A TYPICAL OP-AMP

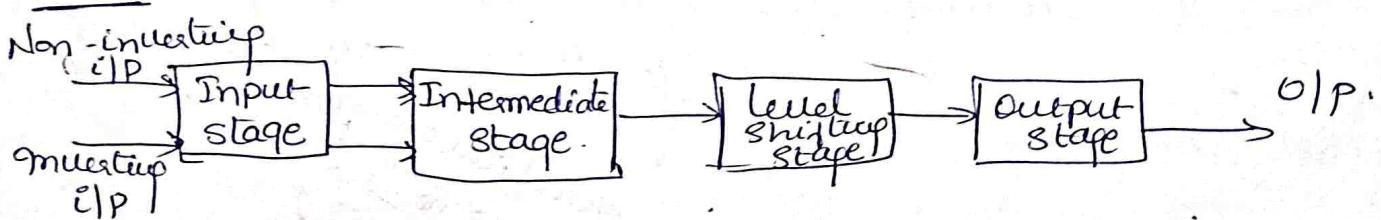

- Block diagram consists of the following stages
- 1. Input stage 2. Intermediate stage 3. Level shifting stage
- 4. Output stage.



1. Input stage is a dual-input, dual output stage. It can handle two inputs - and it provides most of the gain of the op-amp and decides the input impedance of Op-amp.

 - Balanced o/p means, the o/p is zero when two inputs are equal or set to zero.
 - It provides most of the gain of the op-amp and decides the input impedance of Op-amp.


2. Intermediate stage: is a dual-input, unbalanced amplifier.

 - Unbalanced o/p means, the o/p is non-zero, when the two o/p's are equal.
 - Intermediate stage contains one or more differential amplifiers to achieve higher differential gain.


3. LEVEL SHIFTING: It is usually a CC configuration, used to shift the d.c level at the o/p of the intermediate stage downward to zero w.r.t ground.

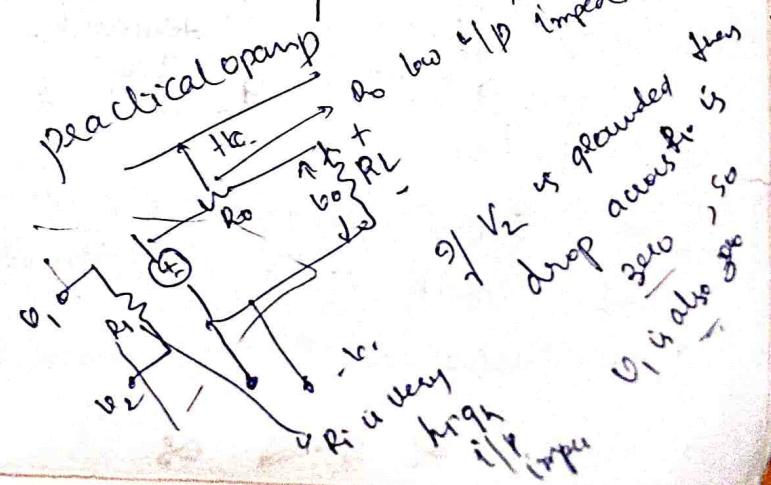4. Output stage: The o/p stage is basically a power amplifier that is used to increase the o/p current supply up capability of the op-amp.

 - It decides the o/p impedance of op-amp.
 - It is desirable to have very low o/p impedance.



CONCEPT OF VIRTUAL SHORT IN AN OP-AMP:

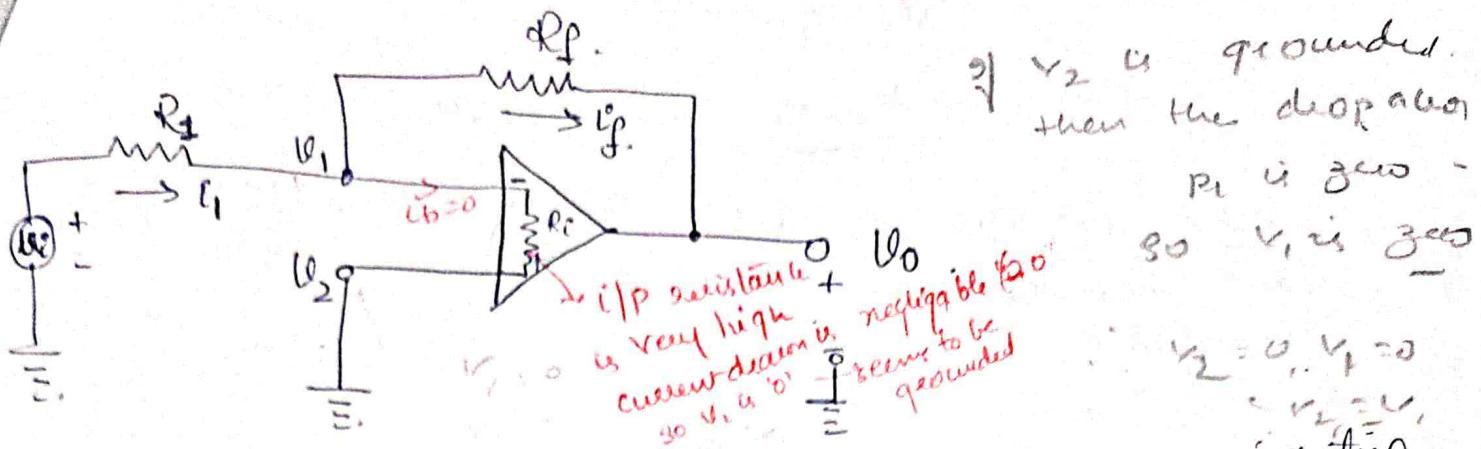

- The above fig shows the circuit of op-amp inverting amplifier which employs 've' of V_b .

- R_i represents the i/p resistance of op-amp measured b/w the inverting and non-inverting i/p terminals.

- The o/p v_{tg} 'V₀' is given by

$$V_0 = A(V_2 - V_1)$$

$$(Q1) \quad V_2 - V_1 = \frac{V_0}{A} \quad \text{--- (1)}$$


- W.R.T where A is the open loop v_{tg} gain of op-amp.

- The o/p voltage 'V₀' cannot exceed the D.C supply v_{tg} given to the op-amp.

[For ex. - for JFET, typically supply v_{tg} is 12V & the open loop gain A is 2×10^5 .]

- To get an o/p v_{tg} of 10V, the required differential i/p v_{tg} is $V_2 - V_1 = \frac{10V}{2 \times 10^5} = 0.5 \mu V$

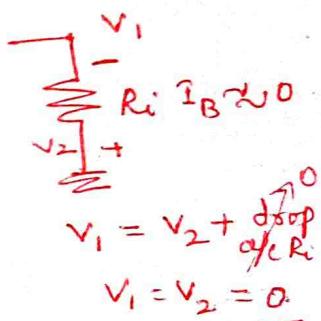→ The value is very small compared to the i/p & o/p voltages.]



- For this reason it is considered as OV The circuit

$$\text{i.e., } V_2 - V_1 \approx 0V \quad (\theta)$$

$$V_2 = 0, V_1 = 0$$

$$\therefore V_2 \approx 0$$


$$V_2 = V_1 \quad \text{---} \quad \textcircled{2}$$

$$V_2 \approx V_1$$

- From Eqn $\textcircled{2}$ we find that the inverting and non-inverting O/P terminals are at the same potential

- i.e., they appear to be shorted.

- \therefore voltage across R_i is zero 

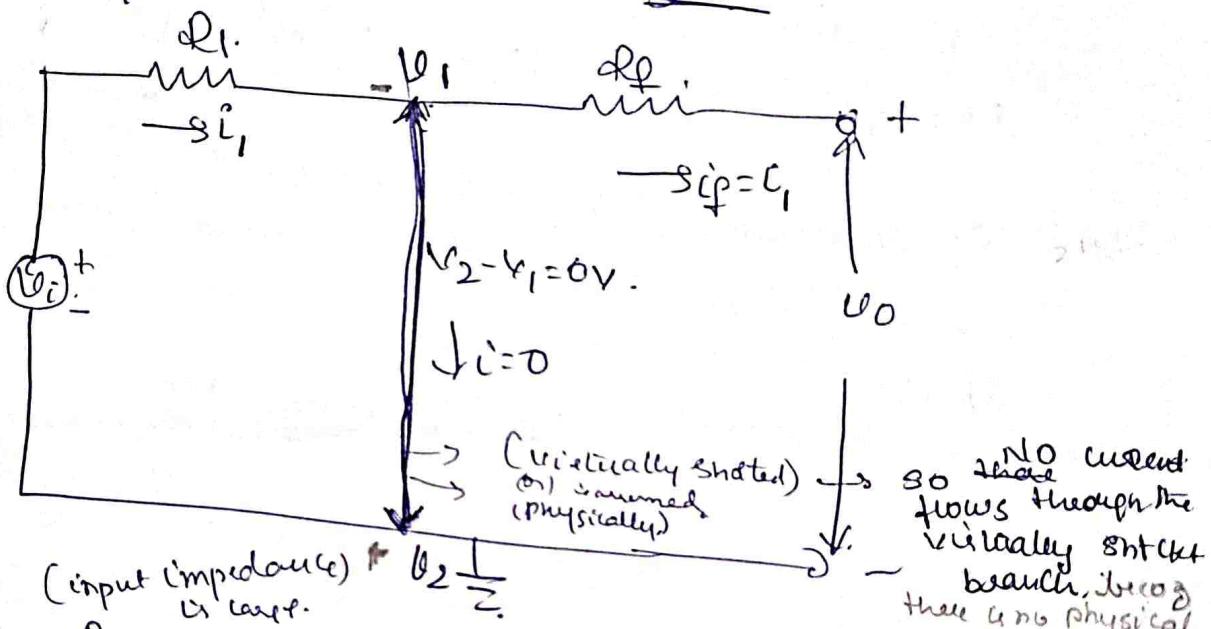

- In O.A. R_i is very large [$2M\Omega$ for 741)] the inverting
current flowing through R_i is almost zero and non-inverting
O/P terminals which are called

- If two terminals are physically shorted, the current flowing through R_i will be zero. virtual and common
As a large current flows through this short.

- Since the voltage b/w the O/P terminals is zero
as no current flows through the short to the ground

Hence we say that as a virtual short exists b/w
the O/P terminals of O/P-aub.

- The virtual short is also called as the virtual
ground

A \rightarrow $\text{Miller's gain of O/P-aub is very large}$
 $\& \text{O/P-gv very low}$ then we say that
the potential at inverting O/P is equal to potential at Non-inverting O/P
i.e. there exists a small voltage between them

(1)

The electrical ground is indicated by thick line b/w the C/P terminals.


(2)

- Note that same current flows through R_1 and R_f

- The concept of virtual short is very much useful in the analysis of Op-amp circuits.

The difference b/w the real short & virtual short is that the current flows b/w two pts which are really shorted but current cannot flow b/w two pts which are virtually shorted. i.e. the concept of virtual gnd is applicable only to op-amp with FB feedback

1. op-amp non-inverting amplifier.

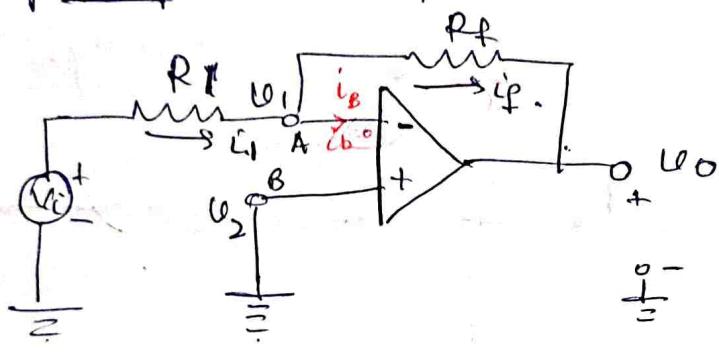

{ '+' terminal
non-inverting }

$$KCL \quad i_f = i_B + i_f^{\text{bias}}$$

$$i_f \approx i_f^{\text{bias}}$$

{ '-' terminal
Non-inverting. }

- Fig shows the circ of an op-amp non-inverting amplifier.
- one C/P signal V_i is applied to the inverting C/P terminal through the resistor R_f .
- Non-inverting C/P terminal is grounded.
- Feed-back from O/P to the inverting C/P terminal is provided through the FB resistor R_f .
- Since the O/P is applied to the inverting C/P terminal, V_O & V_i are of opposite polarity. Hence the FB is -ve.

Since the non-inverting C/P terminal is grounded, $V_2 = 0$

But due to the virtual ground concept at the C/P of op-amp, the inverting & non-inverting C/P terminals are at the same potential
 $\therefore V_1 = V_2 = 0$.

As the i/p impedance of the op-amp is very high, the current flowing into its inverting C/P terminal is zero

\therefore Same current flows through R_i and R_f

$$\text{i.e. } \overset{\circ}{i}_i = \overset{\circ}{i}_f \quad \text{--- (1)}$$

$$\text{But } \overset{\circ}{i}_i = \frac{V_i - V_1}{R_i} = \frac{V_i}{R_i}. \quad \text{--- (2)}$$

$$\& \overset{\circ}{i}_f = \frac{V_1 - V_o}{R_f} = -\frac{V_o}{R_f} \quad \text{--- (3)}$$

Using $\overset{\circ}{i}_i$ in eqn (1) we have

$$\frac{V_i}{R_i} = -\frac{V_o}{R_f}$$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

$$\therefore A_f = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$



$$A_f = -\frac{R_f}{R_i}$$

\Rightarrow where A_f is the closed loop Vtg gain

Note that A_f depends only on the external resistors R_f and $\underline{R_i}$

The i.v.eqn implies that v_o & v_i are of opposite polarity.

waveform

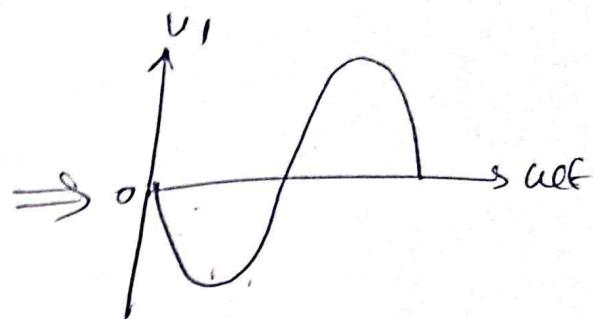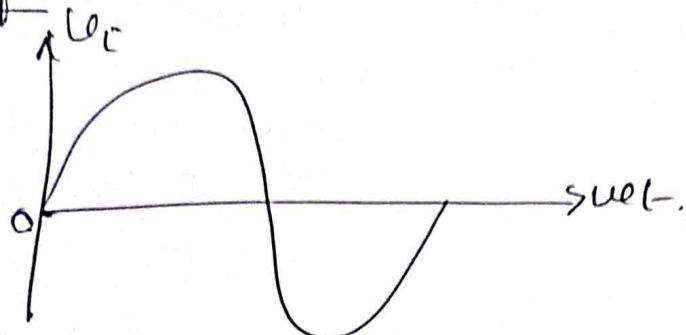

Example 1: A 200 mV peak-to-peak sine waveform v_{tg} is applied to an op-amp inverting amplifier with $\frac{R_f}{R_i} = 10$. Sketch the O/P.

so h peak-to-peak O/P v_{tg}

$$\Delta V_m = 200 \text{ mV}$$



$$|V_m| = 100 \text{ mV}$$

O/P v_{tg} $V_o = V_m \sin \omega t \text{ mV}$


$$V_o = -\frac{R_f}{R_i} \times V_i$$

$$V_o = -10 \times 100 \sin \omega t \text{ mV}$$
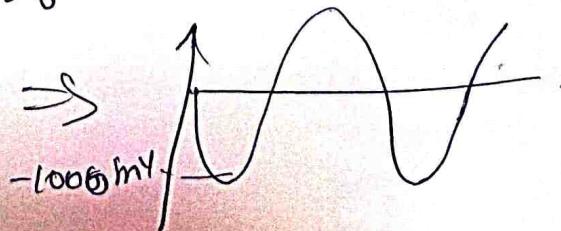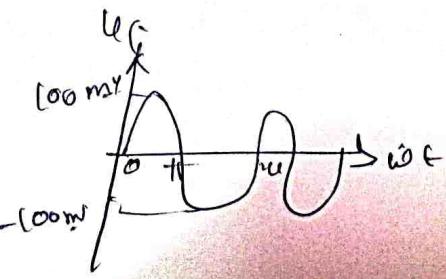
$$V_o = -1000 \sin \omega t \text{ mV} = -3.14159 \dots$$



NOPA Non-Inverting Amplifier

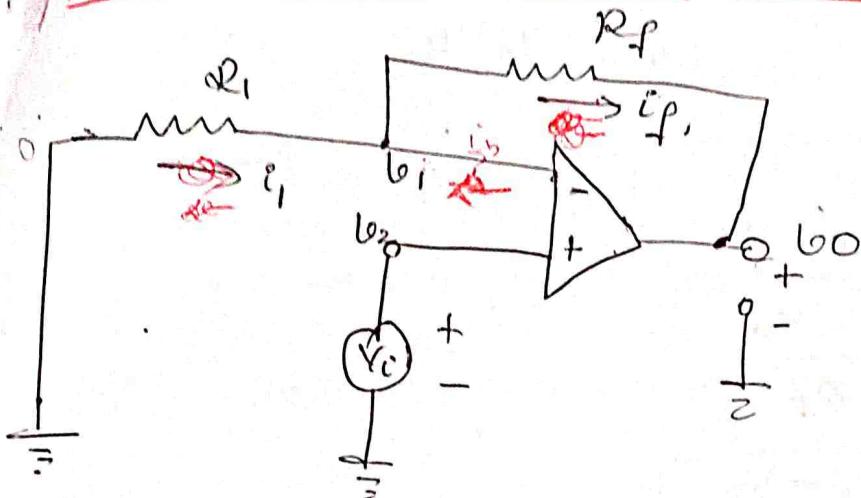

- Feedback resistor 'Rf' appears b/w o/p terminal E_1 & inverting c/p terminal.
- R_1 connects the inverting terminal to ground.
- The c/p signal V_1 is applied at the non-inverting c/p terminal.

$$\therefore V_2 = V_i \quad \text{--- (1)}$$

- W.K.T. Due to virtual ground at the non-inverting c/p of op-amp, the inverting terminals are at the same potential.

$$\therefore V_1 = V_2 \quad \text{--- (2)}$$

Equating eqns (1) & (2)

$$\therefore V_1 = V_i \quad \text{--- (3)}$$

- W.K.T due to high - c/p impedance of op-amp the current flowing into its inverting c/p terminal is zero

- As a result same current flows through R_1, E_1, R_f

$$\therefore i_1 = i_f \quad \text{--- (4)}$$

$$i_1 = \frac{0 - V_i}{R_1} \quad \text{when } V_o = V_i$$

$$\boxed{i_1 = -\frac{V_i}{R_1}} \quad \text{--- 5}$$

$$\text{and } i_f = \frac{V_i - V_o}{R_f}$$

$$\boxed{i_f = \frac{V_i - V_o}{R_f}} \quad \text{--- 6.}$$

using ⑤ & ⑥ in eqn ③.

$$-\frac{V_i}{R_1} = \frac{V_i - V_o}{R_f}$$

$$\frac{V_o}{R_f} = V_i \left[\frac{1}{R_1} + \frac{1}{R_f} \right].$$

$$V_o = V_i R_f \left[\frac{R_f + R_1}{R_1 R_f} \right]$$

$$A_f = \frac{V_o}{V_i} = \left[\frac{R_f}{R_1} + \frac{R_1}{R_f} \right]$$

$$\frac{R_f}{R_1 R_f} + \frac{R_1}{R_1 R_f}$$


$$\underbrace{\frac{V_o}{V_i}}_{\text{closed loop gain}} = 1 + \frac{R_f}{R_1}$$

$$\boxed{A_f = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}}$$

--- ⑦

$\rightarrow A_f$ is the closed loop neg gain or voltage gain with 'f/b'

VOLTAGE FOLLOWER:

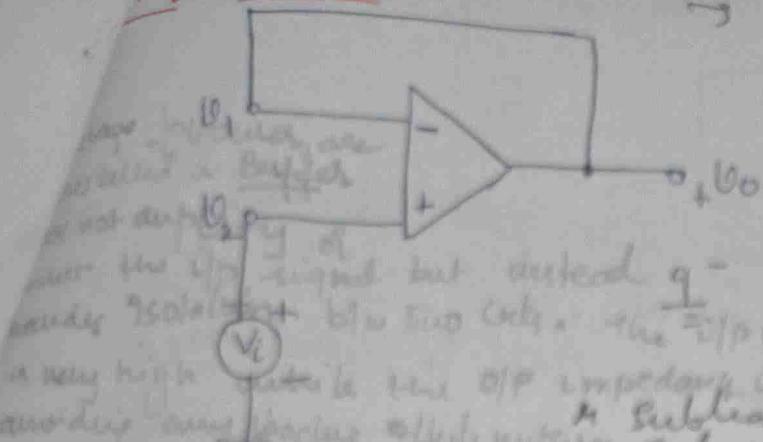


when an op-amp is used for initial applications, the o/p & i/p vtgs are related by a linear law.

some of the basic applications of op-amps are:
 1. Substrates
 2. Integrators
 3. Differentiators
 4. Voltage followers

- A voltage follower is a circuit that isolates the o/p voltage V_o from the i/p voltage V_i .
- Note that the voltage gain of voltage follower is unity — since $V_o = V_i$
- The o/p of voltage follower can be derived from the non-inverting amplifier by shorting coupling R_f & open coupling R_i ,
 i.e., by setting $R_f = 0$ & $R_i = \infty$.
- Since the i/p vtg $\propto eV_i$ is directly applied to the non-inverting i/p terminal.
 $V_o = V_i$ (1)
- Due to initial bias at the i/p of op-amp, the inverting & non-inverting i/p terminals are at the same potential.
 $\therefore V_i = V_2$ (2)
- Note that the inverting i/p terminal is directly tied to the o/p terminal.
 $\therefore V_o = V_i$ (3)

VOLTAGE FOLLOWER:

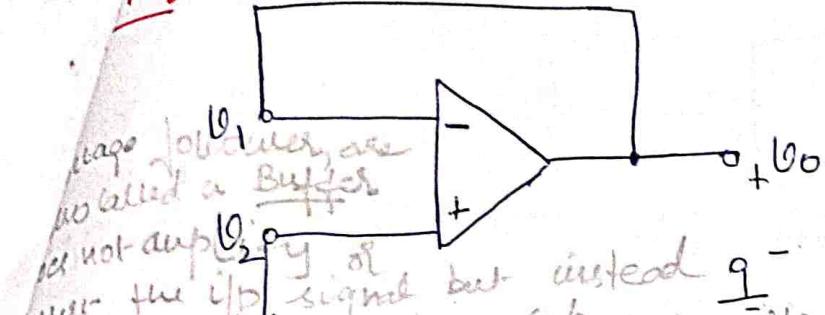

Voltage followers are also called a Buffer
as it not amplifies the input signal but instead gives isolation between inputs. The O/P impedance is very high while the O/P impedance is low.

avoids current loading effects with integral feedback to one of the op-amps, the overall gain of the buffer is +1 and $v_o = v_i$.

- A voltage follower follows the i/p voltage v_i
- Note that the voltage gain of voltage follower is unity — since $v_o = v_i$
- The circuit of voltage follower can be derived from the non-inverting amplifier by shorting circuit R_f & open circuit R_i , i.e., by setting $R_f = 0$ & $R_i = \infty$.
- Since the i/p v/tg v_i is directly applied to the non-inverting i/p terminal. $\therefore v_2 = v_i$ ————— ①
- Due to virtual short at the i/p of op-amp, the inverting & non-inverting i/p terminals are at the same potential — $\therefore v_1 = v_2$ ————— ②

- Note that the inverting i/p terminal tied to the o/p terminal. $\therefore v_o = v_1$ ————— ③

→ when an op-amp is used for special applications, the o/p & i/p v/tgs are related by a factor of 4.

some of the basic applications of op-amps are voltage follower, summing junction, the o/p voltage $v_o = v_i$.

∴ combining all these '3' eqns - we have.

$$\boxed{V_O = V_i} \quad \text{--- (4)}$$


$$V_O = V_1 \\ b_0 = V_2$$

- from eqn (4) we can find that O/P vbg follows the o/p voltage.
- the closed loop vbg gain is given by

$$\boxed{A_f = \frac{b_0}{V_i} = 1} \quad \text{--- (5)}$$

- NOTE that the closed loop vbg gain is unity.

4) OPAMP SUMMER (OR) SUMMING AMPLIFIER:

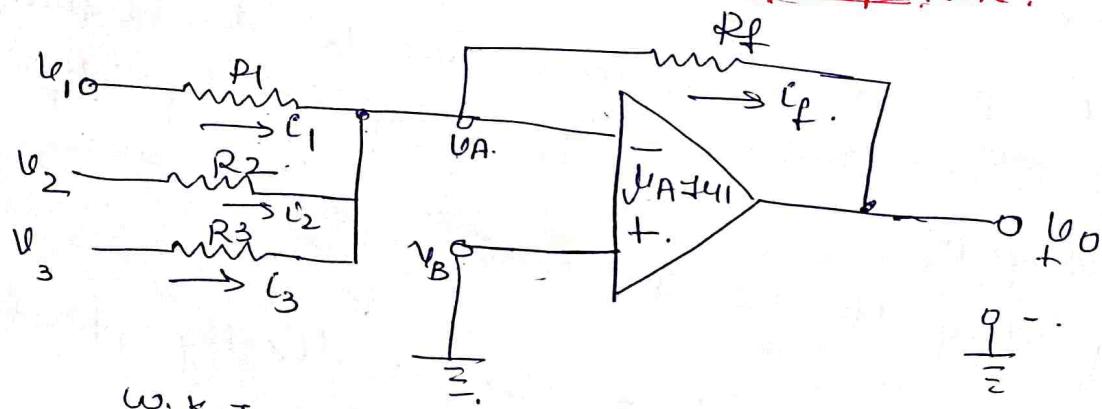

- Since the non-inverting O/P terminal of op-amp is grounded $V_B = 0$.
- Due to virtual short at the O/P of op-amp, the inverting & non-inverting O/P terminal are at the same potential.

$$\therefore V_A = V_B = 0. \quad \text{--- (1)} \quad i_f = C_f$$

$$i_f = i_1 + i_2 + i_3 \Rightarrow [\text{By applying KCL at node A, } i_1 = i_f] \quad \text{--- (2)}$$

$$i_1 = \frac{V_1 - V_A}{R_1} = \frac{V_1}{R_1} \quad \text{--- (3)}$$

$$i_2 = \frac{V_2 - V_A}{R_2} = \frac{V_2}{R_2} \quad \text{--- (4)}$$

③

$$i_3 = \frac{V_3 - V_A}{R_3} = \frac{V_3}{R_3} \quad \text{--- (4)}$$

$$i_f = \frac{V_A - V_o}{R_f} = -\frac{V_o}{R_f} \quad \text{--- (5)}$$

due to the high i/p impedance of the op-amp,
the current flowing into its non-inverting i/p terminal is zero.

Applying Kirchhoff's law

∴ substituting i_1, i_2 & i_3 in (5) we have

$$-\frac{V_o}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\therefore V_o = - \left[\frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} + \frac{R_f V_3}{R_3} \right]$$

∴ if we choose $R_f = R_1 = R_2 = R_3$, then


$$V_o = - \left[\frac{R_1 V_1}{R_1} + \frac{R_2 V_2}{R_2} + \frac{R_3 V_3}{R_3} \right]$$

$$\boxed{V_o = - [V_1 + V_2 + V_3]}$$

Note: that the o/p V_o is equal to the $-ve$ of the sum of the i/p V_{in} 's due to the $-ve$ sign

The circuit is called Summer due to the $-ve$ sign


5) OP-AMP SUBTRACTOR

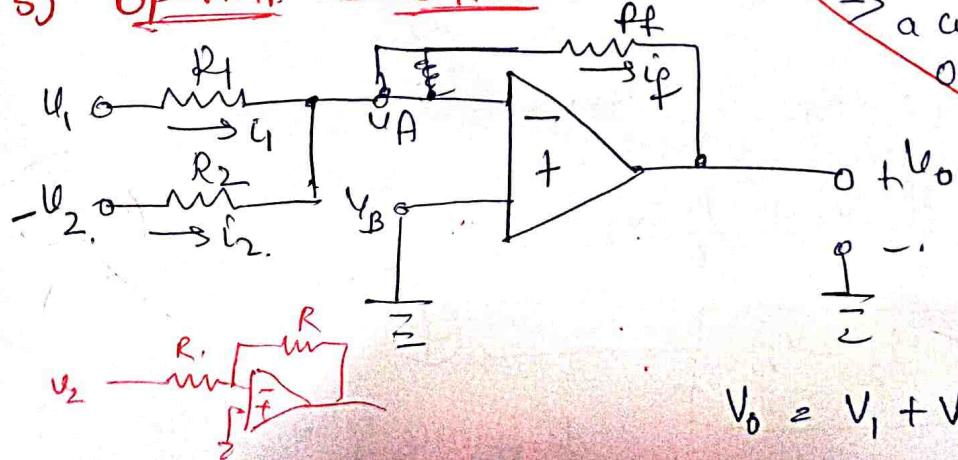

$$V_o = V_1 + V_2 = V_1 - V_2$$

↳ If to Summer circuit, a circuit is designed with op-amp such that its o/p V_o is difference b/w two i/p V_{in} 's. Such circuits are called Subtracter

Op-Amp As HN INTEGRATOR:

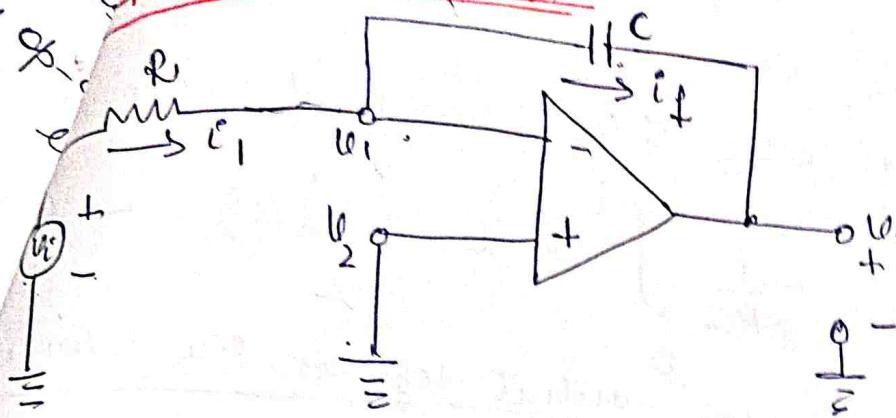

(4)

We want to

Integrator or

$$O/P = \int f(t) dt$$

- Fig shows an op-amp as an integrator. It has a capacitor in the feedback loop.
- Since the non-inverting input terminal of op-amp is grounded $V_2 = 0$.
- Due to virtual short of the input of op-amp, the inverting and non-inverting input terminals are at the same potential.
 $\therefore V_1 = V_2 = 0$. — (1)
- Due to high input impedance of op-amp, the current flowing into its inverting input terminal is zero
~~and~~ ^{law} current flows through R and C.
 $i_{in} = i_f = i_f$ — (2)

$$\text{But } i_1 = \frac{V_i - V_1}{R} = \frac{V_i}{R} \quad (3).$$

$i_p = C \frac{dv_c}{dt} \rightarrow V_c \text{ is the voltage across the capacitor}$

$$\text{and } i_f = C \frac{d}{dt} [V_1 - V_o]$$

$$i_f = -C \frac{dV_o}{dt} \quad (4)$$

Substitute in eqn (1) -

$$\frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$-\frac{V_i}{R} = \frac{dV_o}{dt} \rightarrow \text{integrating both sides}$$

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_C$$

Integrating both sides w.r.t 't' we have


$$V_o = -\frac{1}{RC} \int_0^t V_C dt + V_o(0) \quad \leftarrow \textcircled{3}$$

- where $V_o(0)$ is the initial v_{tg} on the capacitor at $t=0$.
- Note that $V_o(0)$ represents the const of integration.
- From eqn \textcircled{3} we find that the o/p v_{tg} V_o is proportional to the integral of the i/p v_{tg} V_C .
- If the initial v_{tg} on the capacitor at $t=0$, i.e., $V_o(0) = 0$

Now eqn \textcircled{3} can be written as

$$V_o = -\frac{1}{RC} \int_0^t V_C dt \quad \leftarrow \textcircled{6}$$

7) OP-AMP AS DIFFERENTIATOR:

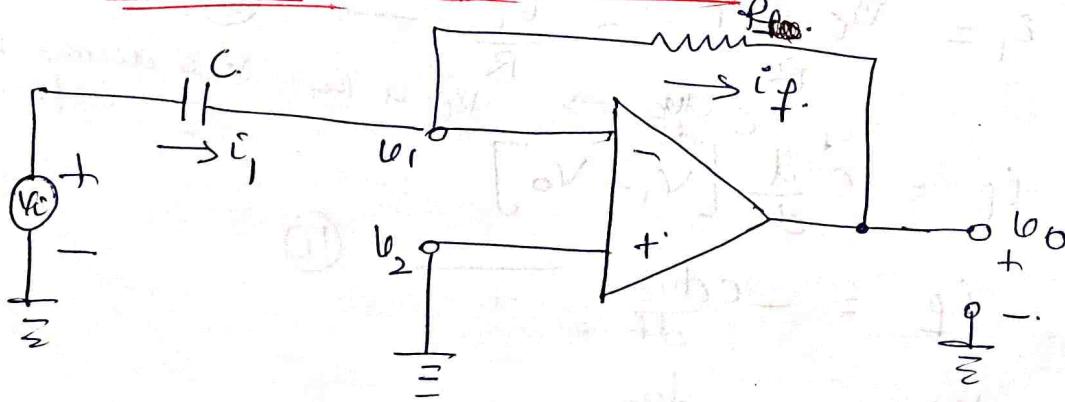

(5) shows the op-amp differentiator.

The circuit of op-amp differentiator can be obtained from op-amp integrator by simply interchanging the positions of 'R' and 'C'.

Since the non-inverting terminal of op-amp is grounded $V_2 = 0$.

Due to the virtual short of the output terminal of op-amp,

the inverting & non-inverting terminals are at the same potential.

$$\therefore V_1 = V_2 = 0 \quad \text{--- (1)}$$

Due to the high input impedance of op-amp, the current flowing into the inverting terminal flows through 'R' and 'C'.

Q 20.

∴ the current flows through $i_1 = i_{if}$. $\quad \text{--- (2)}$

$$\text{But } C_1 = \frac{cd}{dt} [V_i - V_1]$$

$$i_1 = C \frac{dV_i}{dt} \quad \text{--- (3)}$$

$$\text{Eq if } \therefore \frac{V_i - V_o}{R} = -\frac{V_o}{R}. \quad \text{--- (4)}$$

Now Eqs (3) & (4) can be substituted in Eq (2)

$$\frac{cdV_i}{dt} = -\frac{V_o}{R}$$

$$V_o = -RC \frac{dV_i}{dt}$$

$\quad \text{--- (5)}$

∴ it is differentiator Q 3/P

④ Shows the old village in proportion to
the new village.

Old
village

New
village


Old
village

New
village

Old
village

New
village

Opamp - as subt actor

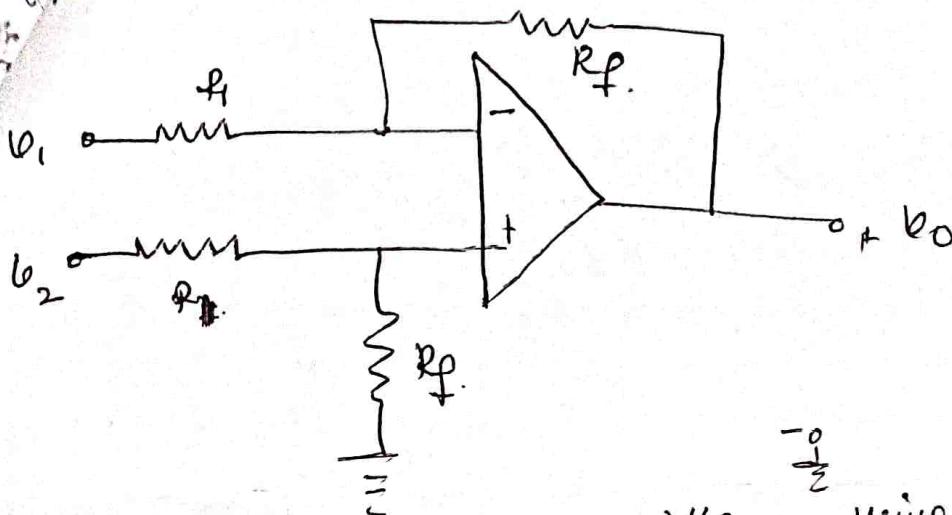


→ let us obtain the o/p vltg V_{O_1} using superposition principle by applying the following steps

Step 1:

V_2 to ground and o/p to V_1

[not opamp but an inverting amplifier]

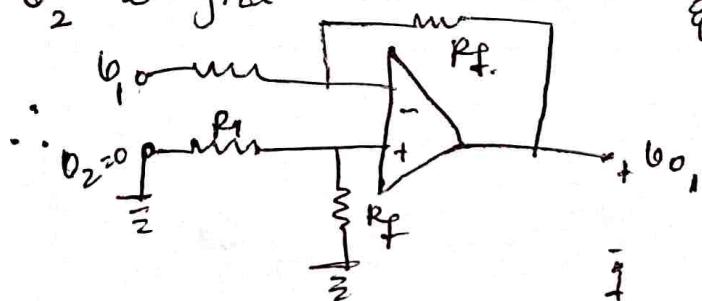


$$\therefore V_{O_1} = -\left[\frac{R_f}{R_1}\right]V_1$$

Step 2:

now V_1 to zero (ground) and find V_{O_2}

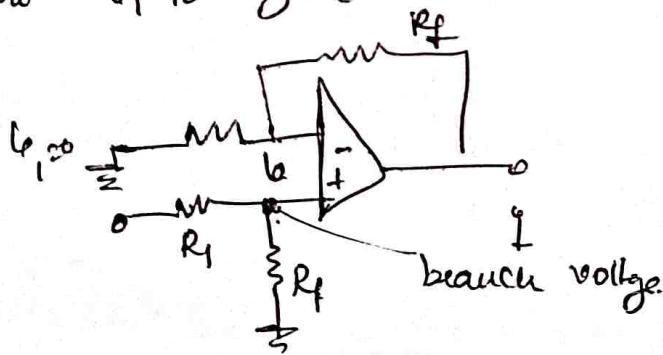[not opamp but an non-inverting amplifier.]



$$V_{O_2} = V \times \text{Gain of non-inverting amplifier}$$

$$= V \times \left[1 + \frac{R_f}{R_1}\right] \quad \text{--- (1)}$$

where 'V' is the voltage drop across R_f . Using voltage division rule

$$V = V_2 \left[\frac{R_f}{R_1 + R_f} \right]$$

$$V = V_2 \left[\frac{R_f}{R_1 \left(1 + \frac{R_f}{R_1}\right)} \right]$$

$$V_{O_2} = V_2 \left[\frac{R_f}{R_1} \right]$$

$$\therefore \text{o/p vltg qu by superposition princpl}$$

$$V_O = V_{O_1} + V_{O_2}$$

$$= -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_1} V_2$$

$$\boxed{V_O = \frac{R_f}{R_1} (-V_2 - V_1)}$$