

Programme: BE	Sem: I	Sec: J to R	CIE: Test 2	Max Marks: 30
Term: 8/8/16 to 17/12/16	Course: Basic Electronics	Code: EC101		Time: 1 Hr date: 12/11/2016

Portions for Test: L13 to L27; Instructions to Candidates: Answer any TWO full Questions

Sl#	Question	Marks	Bloom's Level, and co's
1a)	Define and explain the following (i) CMRR (ii) virtual ground (iii) Input Offset Voltage	5	L1, CO2
1b)	A voltage divider bias circuit has $V_{CC}=18$ volts, $R_1=33$ k ohms, $R_2=12$ kohms, $R_C=1$ kohms, $R_E=1.2$ Kohms, $h_{FE}=50$, given $V_{BE}=0.7$ volts, using find V_E, I_C, V_{CE} and V_C . Draw the DC load line and locate the Q point.	7	L3, CO2
1c)	Perform the following (show the steps) i) $(10.35)_8 = (?)_{10} = (?)_2 = (?)_{16}$	3	L3, CO3
2a)	With neat circuit diagram explain Base Bias method and derive the expression for operating point.	5	L2, CO2
2b)	Design an inverting scaling Adder circuit using an op-amp to give the output voltage $V_O = -(6V_1 + 4V_2 + 15V_3)$. Sketch the designed circuit.	6	L3, CO2
2c)	Perform the following: (i) $(13)_{10} - (86)_{10}$ using 1's complement method (ii) $(1000111)_2 - (10011)_2$ using 2's complement method	4	L3, CO3
3a)	Explain how does op-amp can be used as a Non-inverting amplifier? Derive an expression for voltage gain.	5	L2, CO2
3b)	With neat circuit diagram explain Voltage Divider bias method using approximate analysis?	6	L4, CO2
3c)	Perform the following i) $(16CF.2B)_{16} = (?)_8$ (ii) $(45)_{10} - (8)_{10}$ using 2's complement method OR Determine the base value of x if $(211)_x = (152)_8$	4	L3, CO3