

**EC101/201**

USN 1 M S

M S RAMAIAH INSTITUTE OF TECHNOLOGY

(AUTONOMOUS INSTITUTE, AFFILIATED TO VTU)

BANGALORE - 560 054

SEMESTER END EXAMINATIONS - JANUARY 2016

Course & Branch : **B.E.- Common to all branches** Semester : **I/II**
 Subject : **Basic Electronics** Max. Marks : **100**
 Subject Code : **EC101/201** Duration : **3 Hrs**

Instructions to the Candidates:

- Answer one full question from each unit.

UNIT - I

- Explain the operation of PN diode with basic structure and V-I characteristics. CO1 (06)
 - With neat circuit diagram explain the operation of half wave rectifier with merits and de-merits. CO1 (06)
 - In a Zener regulator the input DC is $10V \pm 20\%$ the output requirements are 5V 20mA, assuming I_{Zmax} and I_{Zmin} as 80mA and 5mA respectively, design a Zener regulator. CO1 (08)
- Define dc-restorer? With relevant diagram explain the positive clamper. CO1 (06)
 - Derive the relation between α_{dc} and β_{dc} . A transistor has $I_B = 100\mu A$, $I_C = 2mA$, find β_{dc} , α_{dc} and I_E . CO1 (06)
 - With neat circuit diagram, illustrate the input and output characteristics of common base configuration. CO1 (08)

UNIT - II

- Why we need biasing? Describe voltage divider biasing with circuit and approximate analysis. CO2 (06)
 - Compare the ideal characteristics of operational-amplifier with practical characteristics. CO2 (06)
 - Describe how op-amp can be used as adder circuit and prove that $V_o = -(V_1 + V_2)$. CO2 (08)
- The base bias circuit is having $R_B = 470K\Omega$, $R_C = 2.2K\Omega$ and $V_{CC} = 20V$, determine I_C , I_B and V_{CE} . When transistor has $h_{FE} = 150$. CO1 (06)
 - With circuit, explain the operation of non-inverting amplifier using op-amp. CO2 (06)
 - Explain how op-amp can be used as integrator with circuit and equations. Write its applications. CO2 (08)

UNIT - III

- Perform the following conversions. CO3 (06)
 i) $(988.8125)_{10} = (?)_{16} = (?)_2$ ii) $(11101010.01011)_2 = (?)_{10} = (?)_8$
 - State and prove the De-Morgan's theorems. CO3 (06)
 - Design half adder combinational logic network using NAND gates only. CO3 (08)
 Using this as a component, draw the circuit for full adder.



6. a) Perform the following. i) $10101001_{(2)} - 10010011_{(2)}$ subtraction using 2's complement method ii) $10111010_{(2)} - 11010101_{(2)}$ subtraction using 1's complement method. CO3 (06)
- b) Discuss the properties of Boolean algebra. CO3 (06)
- c) Simplify the following Boolean expressions and draw the logic circuit using minimum number of gates. CO3 (08)
- i) $Y = a'(b+c')(a+b'+c)(a+b+c)$
- ii) $F = xy + xyz + xyz' + x'yz$

UNIT - IV

7. a) Explain the operation of clocked RS-flip flop with circuit and functional table. CO3 (06)
- b) Compare combinational logic circuit with sequential circuit with example. CO4 (06)
- c) With neat block diagram explain the architecture of 8051 microcontroller architecture. CO4 (08)
8. a) Draw the circuit for simple SR-Latch using NOR gates and explain its operation with functional table and timing diagram. CO3 (06)
- b) Differentiate between microprocessor and microcontroller. CO3 (06)
- c) Discuss the architectural features of 8051 microcontroller with applications. CO3 (08)

UNIT-V

9. a) Explain the need for modulation? Illustrate with example. CO3 (06)
- b) Explain the principle and operation of LVDT with neat sketches. CO1 (06)
- c) Define Amplitude modulation (AM) and derive the necessary equation for AM. CO5 (08)
10. a) Describe the operation of a photo-electric transducer with neat diagram. CO1 (06)
- b) Compare Amplitude Modulation with Frequency Modulation. CO5 (06)
- c) A carrier of 500W, 1MHz is amplitude modulated with sinusoidal signal of 1 KHz, depth of modulation is 60%. Calculate bandwidth, power in the sidebands and total power transmitted. CO5 (08)
